

Assignment1 Extended

Name: Ahmed Nour

Sheet ID: 16

Q1)

Code:

```
module comp (a ,b);
```




```
input [3:0] a;
```

```
output b;
```

```
assign b = (a > 4'b0010 && a < 4'b1000) ? 1 : 0;
```

```
endmodule
```

Simulation:


		Msgs						
 /comp/a  /comp/b		-No Data-	-No Data-					
				4	9	1		

Q2)


To solve the question, we need to divide the clock into the smallest clock of all of them to make sure that there will not be any clock has 0 and 1 at the same moment.

Note: the bold lines are the dividers, the dashed lines test the value at the clock.


a)

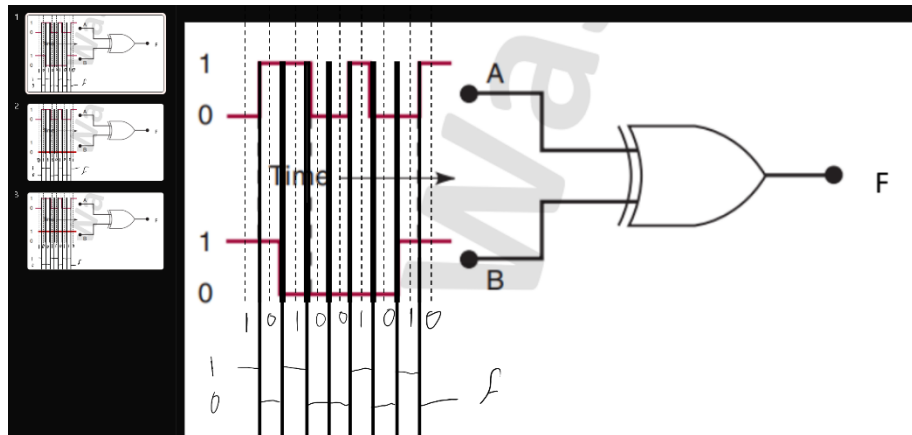

b)

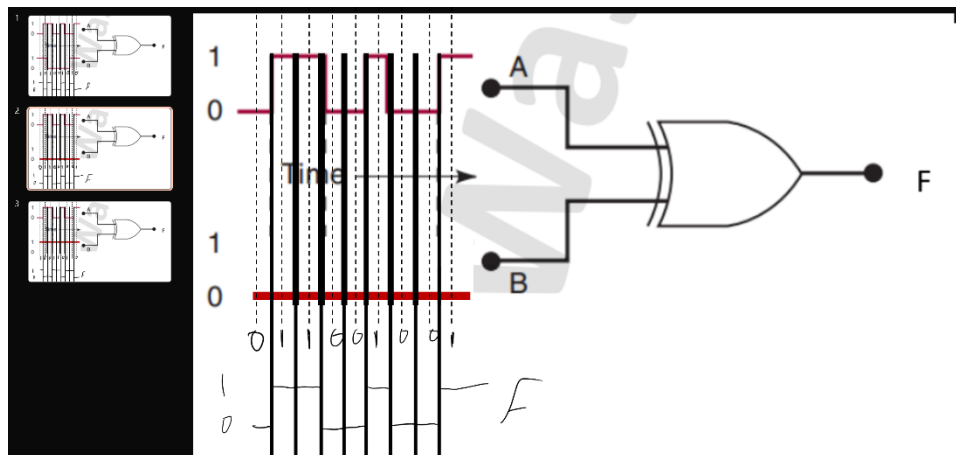

c)

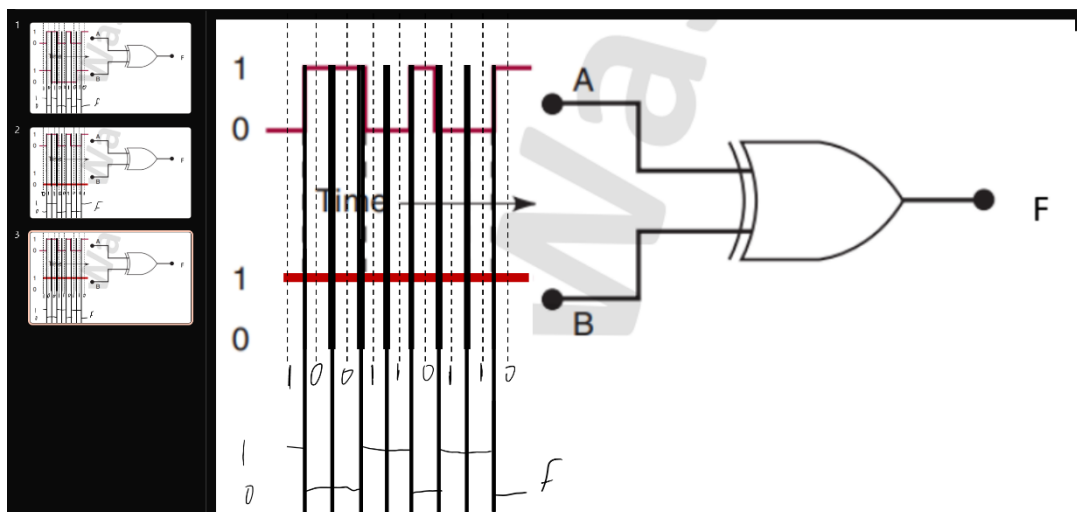

Q3)

Code:

```
module comp (a, b, c, f);
```


```
input a, b, c;
```

```
output f;
```

```
assign f = ((a ^ b) & (b ~^ c) & c);
```

```
endmodule
```

Simulation:

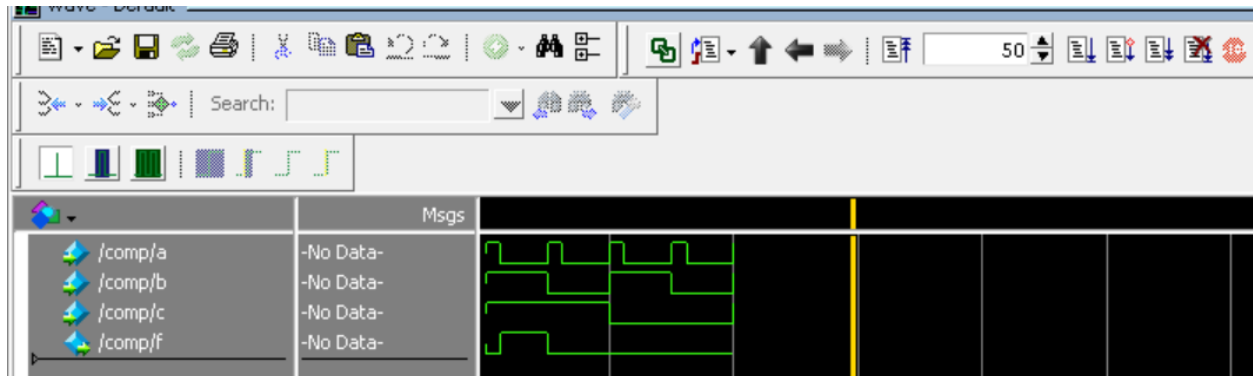


Note: As shown in the simulation the only case that justify $f = 1$ when $a = 0$, $b = 1$ and $c = 1$.

Q4)

Code:

```
module comp (a ,b);  
input [2:0] a;  
output b;  
  
assign b = ~|a;  
  
endmodule
```

Simulation:

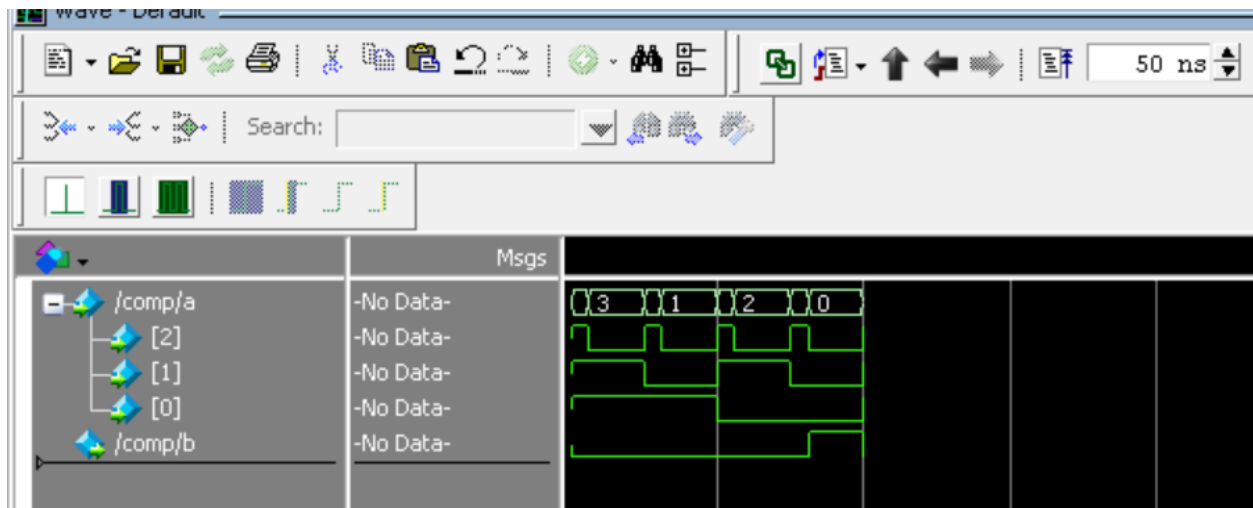

Note: To get 1 only when all bits are 0s and using one gate we use nor due to truth table and the output of the simulation.

A	B	C	X= $\overline{A+B+C}$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Q5)

Code:

```
module ALU1b (a, b, Ainvert, Binvert, CarryIn, Operation, Result, CarryOut);  
    input a, b, Ainvert, Binvert, CarryIn;  
    input [1:0] Operation;  
    output Result, CarryOut;  
  
    wire at, bt;  
  
    assign at = (Ainvert)? ~a : a;  
    assign bt = (Binvert)? ~b : b;  
  
    assign {CarryOut, Result} = (Operation == 0)? (at & bt) : (Operation == 1)? (at | bt) : (at + bt +  
    CarryIn);  
  
endmodule
```

Simulation:

	Msgs								
/ALU1b/a	-No Data-								
/ALU1b/Ainvert	-No Data-								
/ALU1b/b	-No Data-								
/ALU1b/Binvert	-No Data-								
/ALU1b/CarryIn	-No Data-								
/ALU1b/Operation	-No Data-	2			0		1		
/ALU1b/Result	-No Data-								
/ALU1b/CarryOut	-No Data-								